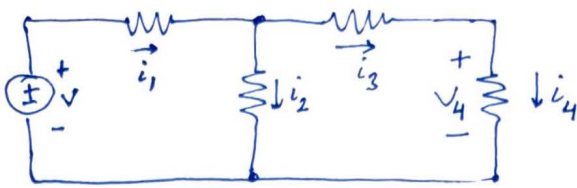


# RESISTIVE NETWORKS

①


A simple electrical network (voltage source + resistors) :



abstract representation of some real electrical network


or  
model of a physical system (heat flow problem in a house)

## Kirchhoff's Current Law (KCL)

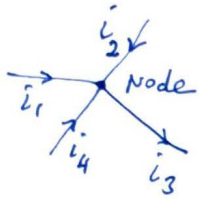

Sum of currents flowing into a common point (node) is  $\phi$ .
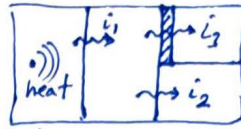
$$\sum i = \phi = i_1 + i_2 - i_3 + i_4$$



Ex.  $i_1 = +5A$ ,  $i_2 = -3A$ ,  $i_4 = +2A$ ,  $\Rightarrow i_3 = ?$


$$+5 - 3 - i_3 + 2 = 0$$

$$i_3 = +4A \checkmark$$

## Kirchhoff's Voltage Law (KVL)

Sum of the voltages around a loop at any instant is zero.

$$\sum v = \phi$$

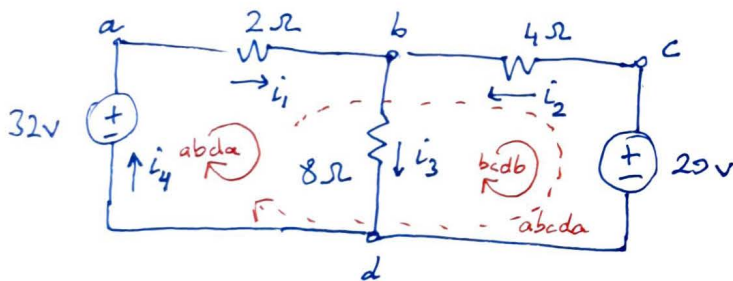

① Apply KCL to node a :

$$\sum i_a = 0 = i_4 - i_1$$

$$i_1 = i_4$$

Current is the same at every point in a series circuit

③ Apply KCL to node b and d

$$\sum i_b = 0 = +i_1 + i_2 - i_3$$

$$\sum i_d = 0 = i_3 - i_4 - i_2 = i_3 - i_1 - i_2$$

$$v = R \cdot i \Rightarrow \begin{aligned} v_{ab} &= +2i_1 \quad (\text{or } v_{ba} = -2i_1) \\ v_{bd} &= +8i_3 & v_{db} &= -8i_3 \\ v_{cb} &= +4i_2 & v_{bc} &= -4i_2 \end{aligned}$$

④ Apply KVL to loop abda, bcd b:

$$\sum v = 0 = v_{ba} + v_{db} + v_{ad} \Rightarrow$$

$$\sum v = 0 = v_{cb} + v_{dc} + v_{bd} \Rightarrow$$

$$0 = -2i_1 - 8i_3 + 32$$

$$0 = +4i_2 - 20 + 8i_3$$

⑤ Apply KVL to loop abcda :

$$\sum v = 0 = v_{ba} + v_{cb} + v_{dc} + v_{ad}$$


$$\begin{aligned} i_1 + i_2 - i_3 &= 0 \\ +2i_1 + 8i_3 &= 0 \\ +4i_2 + 8i_3 &= 0 \end{aligned} \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{Solve!} \rightarrow$$

R.N.

$$A \cdot x = b, \quad A = \begin{bmatrix} 1 & 1 & -1 \\ 2 & 0 & 8 \\ 0 & 4 & 8 \end{bmatrix}, \quad x = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}, \quad b = \begin{bmatrix} 0 \\ 32 \\ 20 \end{bmatrix} \quad (2)$$

→ Solution by determinants, substitution method, Node-voltage (\*)

Node-voltage method:

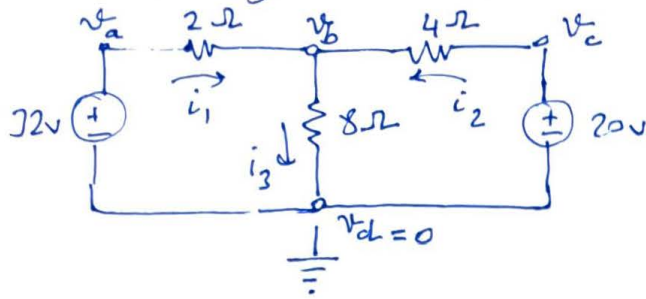

$$\text{KCL to } b: \sum i_b = 0 = i_1 + i_2 - i_3$$

$$i_1 = \frac{v_a - v_b}{2} = \frac{32 - v_b}{2}$$


$$i_2 = \frac{v_c - v_b}{4} = \frac{20 - v_b}{4}$$

$$i_3 = \frac{v_b - 0}{8}$$

$$\Rightarrow 0 = \frac{32 - v_b}{2} + \frac{20 - v_b}{4} - \frac{v_b}{8} \Rightarrow 128 - 4v_b + 40 - 2v_b - v_b = 0$$


$$v_b = \frac{168}{7} = 24 \text{ V} \quad i_3 = \frac{24}{8} = 3 \text{ A} \quad i_1 = \frac{32 - 24}{2} = 4 \text{ A}, \quad i_2 = \frac{20 - 24}{4} = -1 \text{ A}$$

Examples:

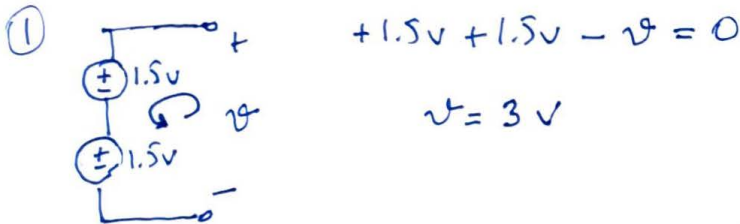

$$+1.5\text{V} + 1.5\text{V} - v = 0$$

$$v = 3\text{V}$$

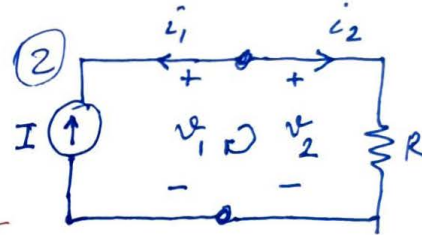

$$i_1 = -I$$

$$v_2 = R i_2$$

$$i_1 + i_2 = 0$$

$$v_2 - v_1 = 0$$


$$v_1 = v_2 = RI$$

④ Power into the current source:

$$i_1 v_1 = -RI^2$$

Power into the resistor
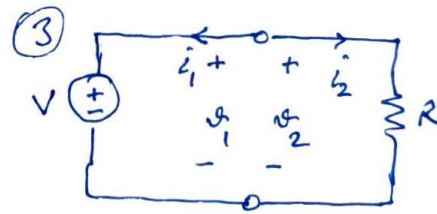
$$i_2 v_2 = RI^2 = R \frac{v^2}{R^2} = \frac{v^2}{R}$$




$$v_1 = V$$

$$v_1 = v_2$$

$$i_1 + i_2 = 0$$


$$v_2 = R \cdot i_2$$
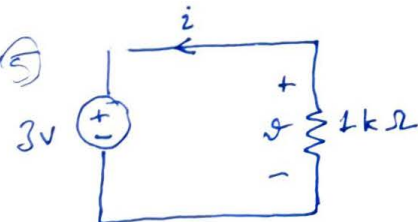
$$-i_1 = i_2 = \frac{V}{R}, \quad v_1 = v_2 = V$$



$i = 3 \text{ mA}$  is correct?

energy dissipated by R is  $i^2 \cdot R = 9 \text{ mW}$   
 energy into the source is  $3\text{V} \cdot 3 \text{ mA} = 9 \text{ mW}$   
 it should be  $-9 \text{ mW} \Rightarrow i$  must be  $-3 \text{ mA}$

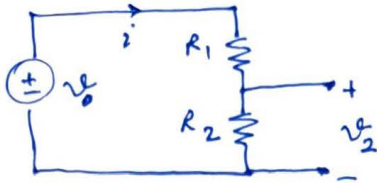Voltage Divider

$$i = \frac{v_0}{R_1 + R_2}, \quad v_2 = R_2 \cdot i = R_2 \frac{v_0}{R_1 + R_2}$$

$$v_2 = \frac{R_2}{R_1 + R_2} \cdot v_0$$

In terms of conductance ( $G = \frac{1}{R}$ ):  $v_2 = \frac{G_1}{G_1 + G_2} \cdot v_0$


Ex.  $v_0 = 10\text{ V}$ ,  $R_2 = 1\text{ k}\Omega$ . Choose  $R_1$  such that  $v_2$  is 10% of  $v_0$ .

$$v_2 = \frac{R_2}{R_1 + R_2} \cdot v_0 \Rightarrow \frac{v_2}{v_0} = 0.1 = \frac{1\text{ k}\Omega}{R_1 + 1\text{ k}\Omega} \Rightarrow R_1 = 9\text{ k}\Omega$$

Resistors in series:




N-Resistor Voltage Divider:

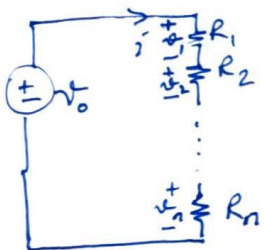


$$-v_0 + v_1 + \dots + v_n = 0$$

$$i = \frac{v_0}{R_1 + R_2 + \dots + R_n}$$

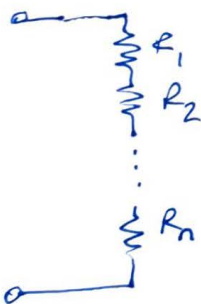
$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_n} \cdot v_0$$



equivalence

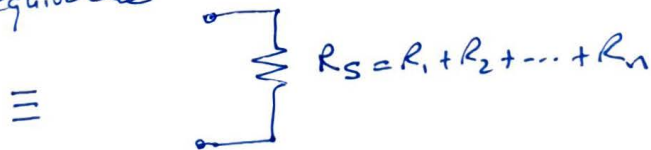

Example:

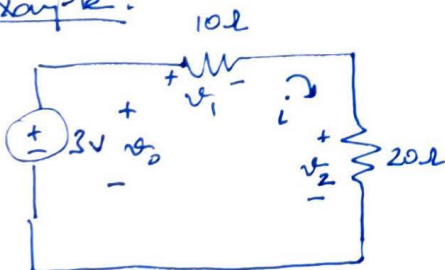

$$i = \frac{3}{30} = 0.1\text{ A}$$


$$v_1 = R_1 i = 10 \cdot 0.1 = 1\text{ V}$$

$$v_2 = R_2 i = 20 \cdot 0.1 = 2\text{ V}$$



# R.N. Resistors in Parallel:

(4)

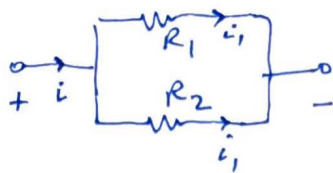

$$i = i_1 + i_2$$

$$i_1 = \frac{V_0}{R_1}$$

$$i_2 = \frac{V_0}{R_2}$$

$$V_0$$

||| equiv.

$$i = \frac{V_0}{R_p} = \frac{V_0}{R_1} + \frac{V_0}{R_2} \Rightarrow \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$\text{or } R_p = \frac{R_1 R_2}{R_1 + R_2} //$$


we use sometimes this notation:

$$R || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


for n resistor case:  $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$

for n resistor equal ( $R_i = R \forall i$ ):  $R_p = \frac{R}{n} //$

Equivalent resistors:

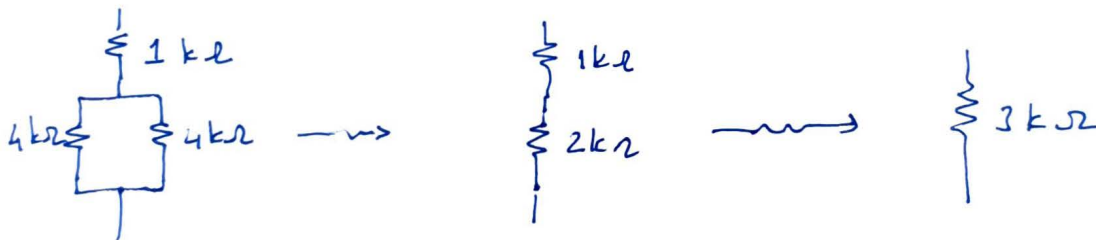

More complex example:

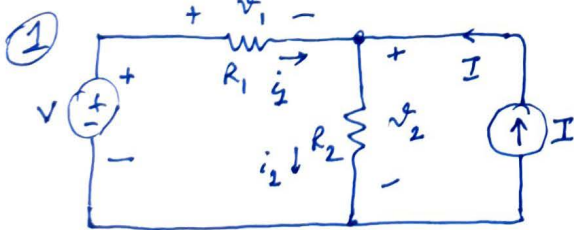


$$I \neq i_1 = i_2 \quad i_2 = \frac{V_2}{R_2} \quad i_1 = \frac{V - V_2}{R_1}$$

$$\frac{I}{(R_1 R_2)} + \frac{V - V_2}{(R_1 R_2)} = \frac{V_2}{(R_2)} \Rightarrow$$

$$I R_1 R_2 + V R_2 - V_2 R_2 = V_2 R_1$$

$$I R_1 R_2 + V R_2 = V_2 (R_1 + R_2) \Rightarrow V_2 = \frac{I R_1 R_2 + V R_2}{R_1 + R_2}$$

$$i^2 R = 9 \times 3 = 27 \text{ W}$$

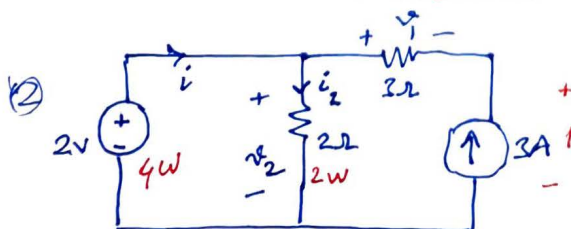

$$V_2 = \frac{R_1 R_2}{R_1 + R_2} I + \frac{R_2}{R_1 + R_2} V //$$

$$-i_2 + i + 3 = 0 \Rightarrow i = -2 \text{ A}$$

$$i_2 = \frac{2}{2} = 1 \text{ A}$$

Power dis. in resistors: 29 W

Power into sources:

$$-11 \text{ V} \cdot 3 \text{ A} + 2 \text{ V} \cdot 2 \text{ A} = -29 \text{ W}$$

Show the energy conservation!