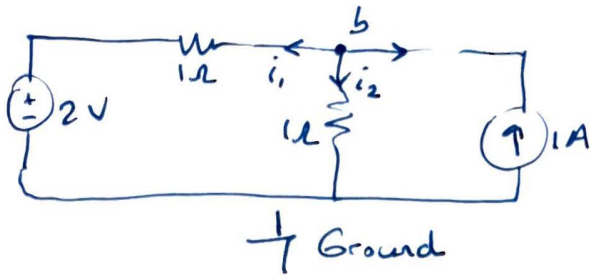


NETWORK THEOREMS

(1)


Node Voltage



$$\frac{v_b}{1} + \frac{v_b - 2}{1} - 1 = 0 \Rightarrow v_b = 1.5 \text{ V}$$


$$i_1 = \frac{1.5 - 2}{1} = -0.5 \text{ A}$$

$$i_2 = \frac{1.5}{1} = 1.5 \text{ A}$$

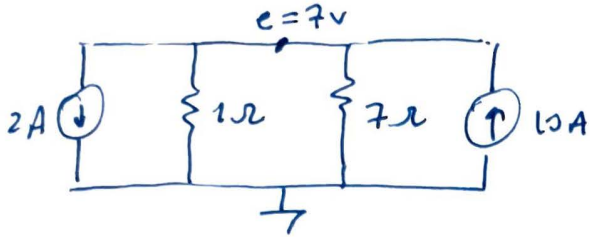

show node voltage $e = 7\text{V}$ satisfies KCL.
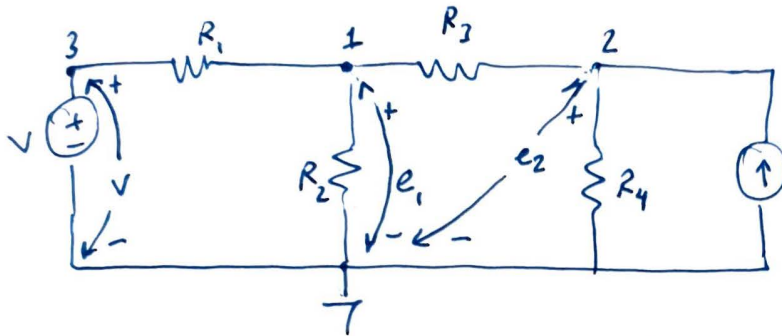
$$2\text{A} + \frac{(7-0)\text{V}}{1\Omega} + \frac{(7-0)\text{V}}{7\Omega} - 10\text{A} = 0$$




$$\text{KCL: } \frac{v - e_1}{R_1} + \frac{e_2 - e_1}{R_3} - \frac{e_1}{R_2} = 0$$

$$\text{Node 2: } \frac{e_1 - e_2}{R_3} - \frac{e_2}{R_4} + I = 0$$

$$\frac{V}{R_1} = e_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{e_2}{R_3}$$

$$I = -\frac{e_1}{R_3} + e_2 \left(\frac{1}{R_3} + \frac{1}{R_4} \right)$$

Example

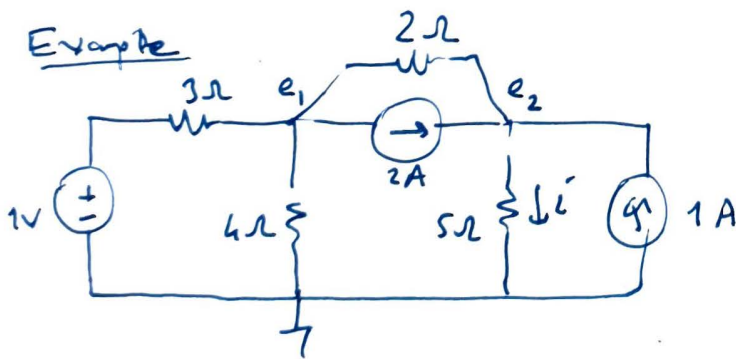


$$\frac{e_1 - 1}{3} + \frac{e_1}{4} + \frac{e_1 - e_2}{2} + 2 = 0$$

$$-2 + \frac{e_2 - e_1}{2} + \frac{e_2}{5} - 1 = 0$$

$$e_1 = 0.65 \text{ V}$$

$$e_2 = 4.75 \text{ V} \Rightarrow i = \frac{4.75}{5} = 0.95 \text{ A}$$

example


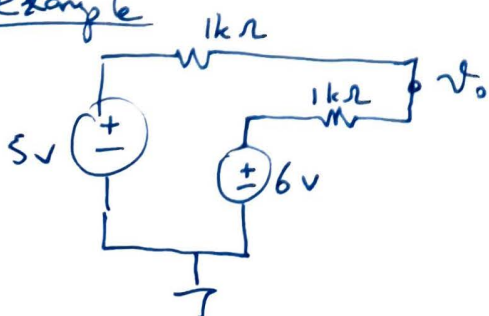


$$\frac{v_o - 5}{1} + \frac{v_o - 6}{1} = 0 \Rightarrow v_o = 5.5 \text{ V}$$


* V_{TH} can be found by calculating open-circuit voltage at the designated terminal pair.

* R_{TH} can be found by calculating the resistance of the open-circuit network seen from the designated terminal pair.



(Ex.)

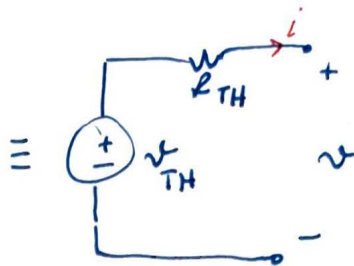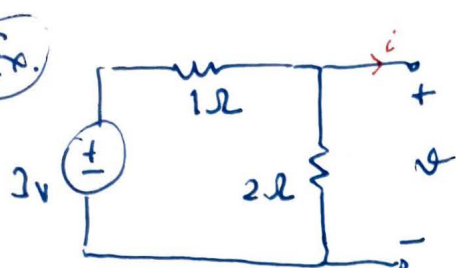
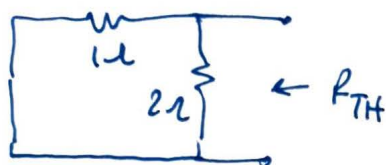
$$V_{TH} = 3V \cdot \frac{2\Omega}{1\Omega + 2\Omega} = 2V$$



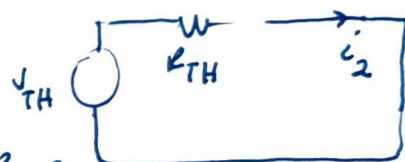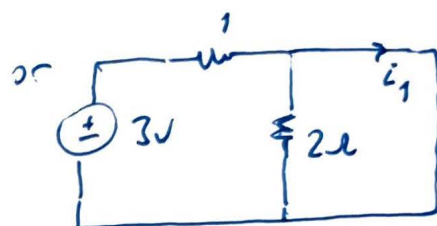
$$R_{TH} = 1 \parallel 2 = \frac{2}{3} \Omega$$





$$i_1 = i_2$$

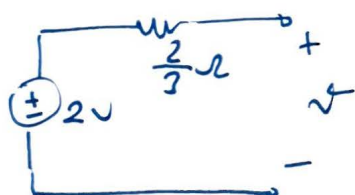
$$3 = \frac{V_{TH}}{R_{TH}} = 2 \Rightarrow R_{TH} = \frac{2}{3} \Omega$$






(Ex.)

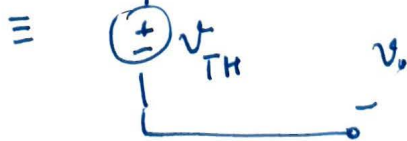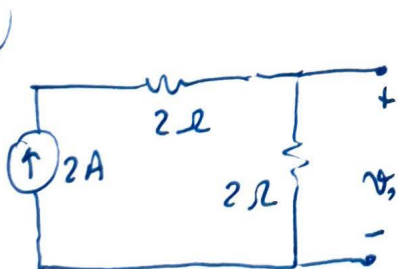

$$V_{TH} = 2A \cdot 2\Omega = 4V$$

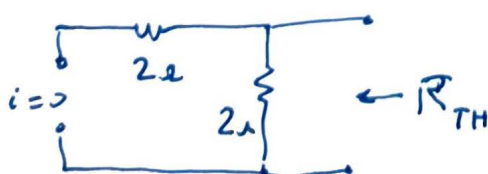

$$\Rightarrow R_{TH} = 2\Omega$$

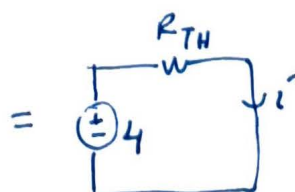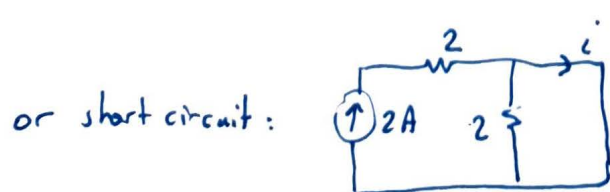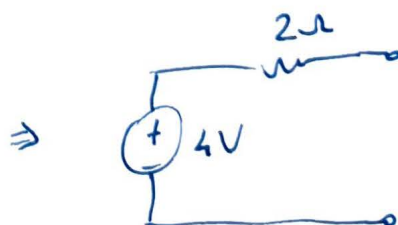


$$i = 2 = \frac{4}{R_{TH}} \Rightarrow R_{TH} = 2\Omega$$

$$i = 2$$



N.T.

(4)

Ex.

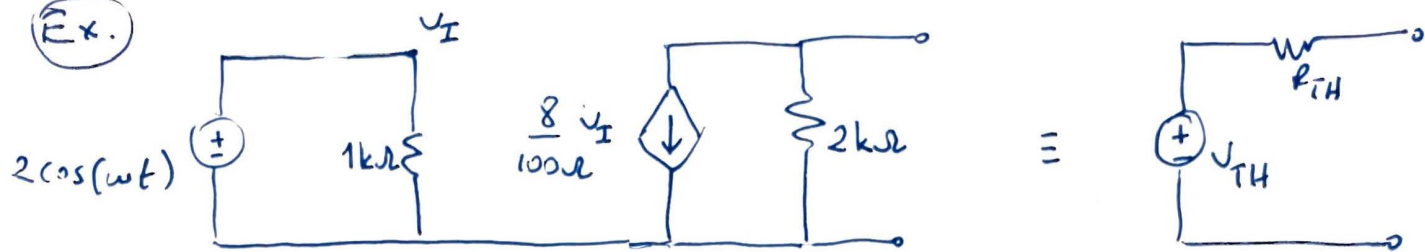

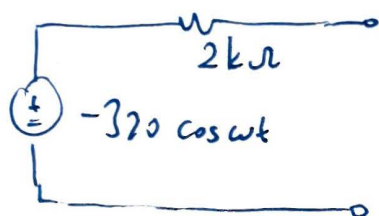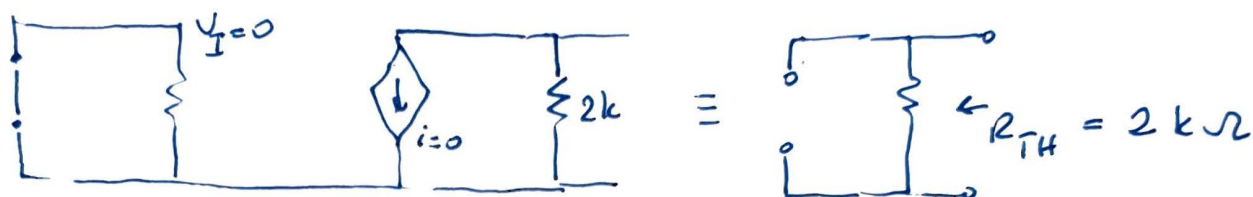
$$- V_{TH} = \underbrace{2\cos(\omega t)}_{v_I} \cdot \frac{8}{100} \cdot 2k\Omega = 320 \cos(\omega t)$$



NON - LINEAR CIRCUITS

(1)

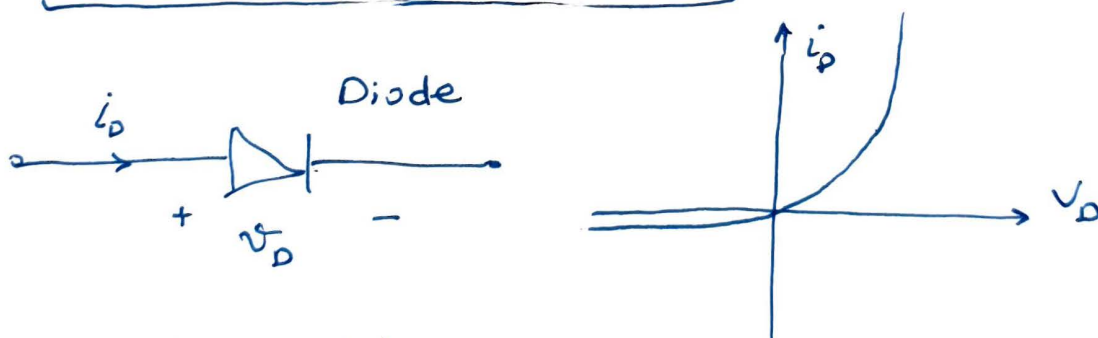

$$i_D = I_S (e^{v_D/V_{TH}} - 1) \text{ where } V_{TH} = 0.025V, I_S = 10^{-12}A$$

Question: Determine the value of i_D for $v_D = 0.5, 0.6$ and 0.7 ?

$$i_D = 10^{-12} \cdot (e^{0.5/0.025} - 1) = 0.49 \text{ mA}$$

$$0.6 \Rightarrow 26 \text{ mA}$$


$$0.7 \Rightarrow 1450 \text{ mA}$$

} dramatic increase

NON-LINEAR CIRCUITS

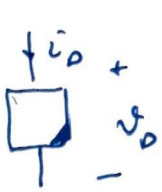
(2)

Another non-linear device: (Hypothetical)




$$i_D = \begin{cases} 0.1 v_D^2 & v_D \geq 0 \\ 0 & v_D < 0 \end{cases}$$

Example:

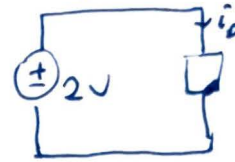

$$i_D = 0.1 \cdot 2^2 = 0.4 \text{ A}$$

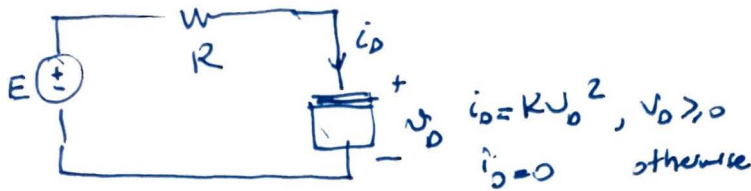

$$i_D = K v_D^2, v_D \geq 0$$


$$i_D = 0 \text{ otherwise}$$

$$\frac{v_D - E}{R} + i_D = 0$$


$$\frac{v_D - E}{R} + K v_D^2 = 0$$

$$R K v_D^2 + v_D - E = 0$$

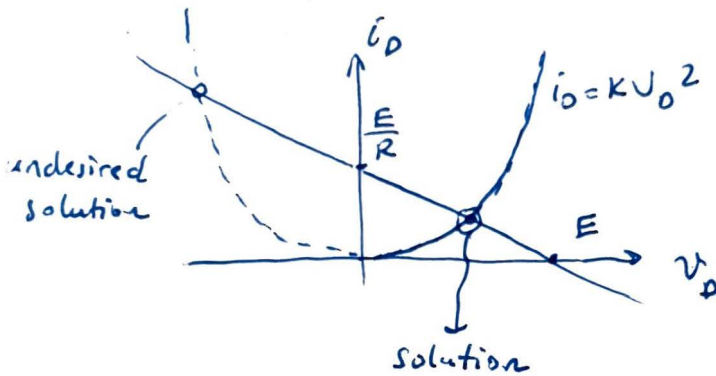
$$v_D = \frac{-1 + \sqrt{1 + 4 R K E}}{2 R K}$$




Example:

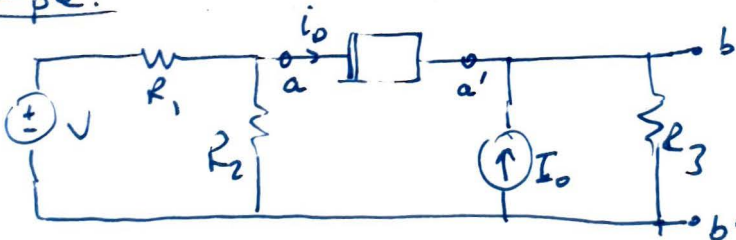

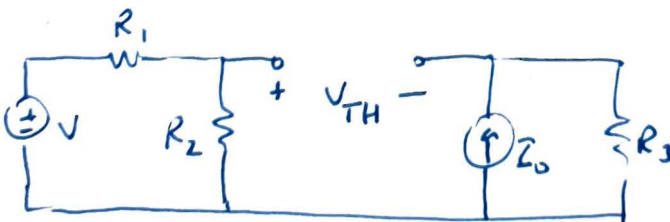Perform Thevenin analysis:
(Terminals a-a')


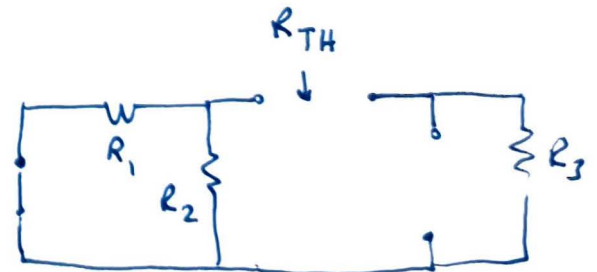
$$V_{TH} = V \frac{R_2}{R_1 + R_2} - I_0 R_3$$



$$R_{TH} = (R_1 \parallel R_2) + R_3$$

Question: Can you find Thevenin equivalent at terminals b-b'?