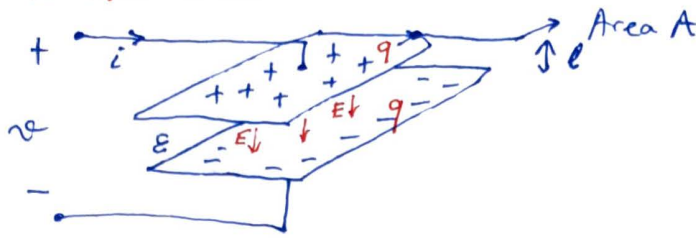


ENERGY STORAGE ELEMENTS

(1)

Time has not been taken into account so far. Capacitive and inductive effects change this.

Capacitor



The charge accumulates on plates. (+, - charge on each plates). There is electric field between plates

$$E(t) = \frac{q(t)}{\epsilon A(t)}, \quad v(t) = l(t) \cdot E(t)$$

ϵ = dielectric permittivity for insulator.

$$\text{so } q(t) = \frac{\epsilon A(t)}{l(t)} \cdot v(t) = C(t) v(t)$$

C : capacitance (Coulombs / Volt : Farad (F))

Resistor exhibits proportional relation between current and voltage.

capacitor exhibits proportional relation between voltage and stored charge.


Rate of charge transfer is current : $\frac{dq(t)}{dt} = i(t)$ (Coulomb/second : Ampere)

$C(t)$ capacitance is usually time invariant : C


* Stores electric field !

$$q(t) = C v(t)$$
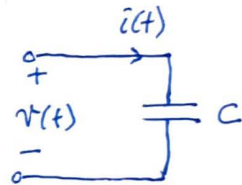
$$i(t) = C \frac{dv(t)}{dt} \quad \text{or} \quad v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$



Inductor

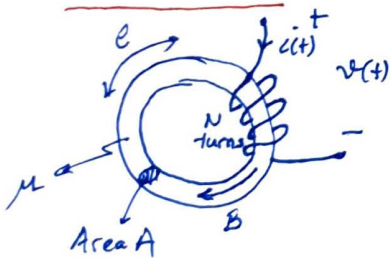

$$B(t) = \frac{\mu N i(t)}{l(t)}$$

↓
density of flux

$$\Phi(t) = A(t) \cdot B(t)$$

↓
magnetic flux

$$\lambda(t) = N \Phi(t) = \frac{\mu N^2 A(t)}{l(t)} i(t)$$

↓
total flux

$L(t)$


L : inductance (Webers / Ampere : Henry (H))

$L(t)$ is usually time invariant : L .

$$\frac{d\lambda(t)}{dt} = v(t)$$

* Stores magnetic field !

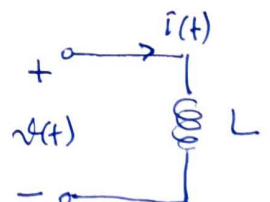
$$v(t) = L \frac{di(t)}{dt} \quad \text{or} \quad i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt$$



ENERGY STORAGE ELEMENTS

2


Series and Parallel Connections

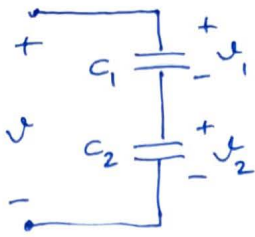

$$q(t) = C_1 v_1(t) + C_2 v_2(t)$$

$$v(t) = v_1(t) + v_2(t)$$
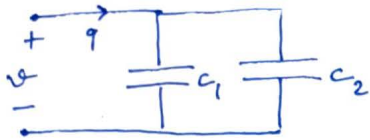
$$\frac{1}{C} = \frac{v(t)}{q(t)} = \frac{1}{C_1} + \frac{1}{C_2}, \quad C = \frac{C_1 C_2}{C_1 + C_2}$$





$$v(t) = \frac{q_1(t)}{C_1} = \frac{q_2(t)}{C_2}$$

$$q(t) = q_1(t) + q_2(t)$$

$$C = \frac{q(t)}{v(t)} = C_1 + C_2$$


Ex.

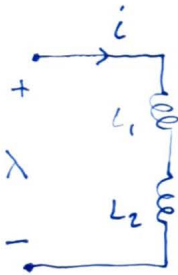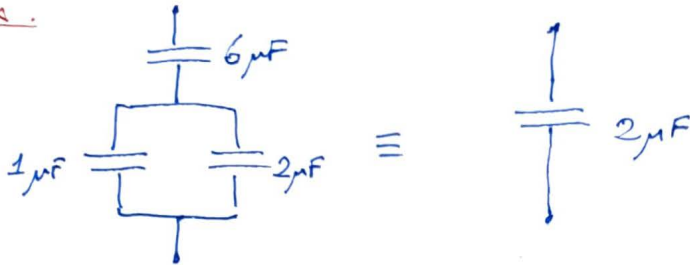

$$i(t) = \frac{\lambda_1(t)}{L_1} = \frac{\lambda_2(t)}{L_2}$$



$$\lambda(t) = \lambda_1(t) + \lambda_2(t)$$
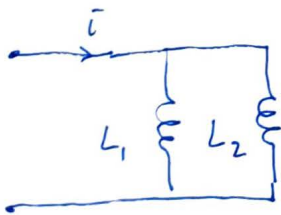
$$L = \frac{\lambda(t)}{i(t)} = L_1 + L_2$$



Similarly, $\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} \Rightarrow L = \frac{L_1 \cdot L_2}{L_1 + L_2}$

TRANSFORMERS

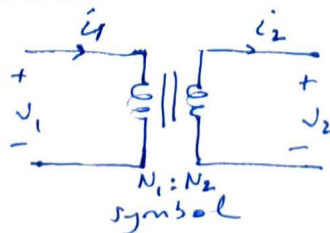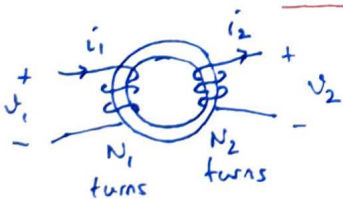

$$v_1 = N_1 \frac{d\phi(t)}{dt}$$

$$v_2 = N_2 \frac{d\phi(t)}{dt}$$

$$\frac{v_1(t)}{N_1} = \frac{v_2(t)}{N_2}$$

$$N_1 i_1(t) = N_2 i_2(t)$$