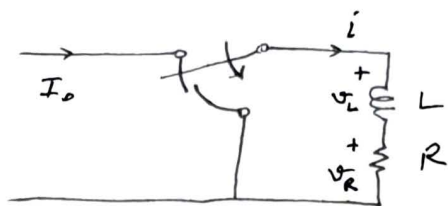


FIRST-ORDER CIRCUITS/SYSTEMS

①


The highest degree of derivative is 1. \rightarrow RC, LR networks:

L-R example:



$$\text{KVL: } \sum v = 0 = -v_L - v_R = -L \frac{di}{dt} - Ri$$

$$L \frac{di}{dt} + Ri = 0$$

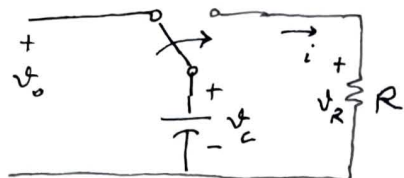

$$\text{KVL: } \sum v = 0 = v_C - v_R = v_0 - \frac{1}{C} \int i dt - Ri$$

$$R \frac{di}{dt} + \frac{1}{C} i = 0$$

Analogy with mechanics:



D : coefficient of friction. Driving force is removed at $t=0$.
At $t=0$, $v = v_0$.

$$\rightarrow v (v_0 \text{ at } t=0)$$

$$\sum f = 0 = -m \frac{dv}{dt} - Dv$$

$$m \frac{dv}{dt} + Dv = 0$$

Solving the Equation:

$R \frac{di}{dt} + \frac{1}{C} i = 0$ says that combination of $i(t)$ and $\frac{d}{dt} i(t)$ must equal zero.

This is possible if the function is exponential.

$$i = A e^{st} \Rightarrow \frac{di}{dt} = s A e^{st} \quad R s A e^{st} + \frac{1}{C} A e^{st} = 0$$


$$\left(\underbrace{Rs + \frac{1}{C}}_0 \right) A e^{st} = 0$$

$$s = -\frac{1}{RC} \quad \text{Therefore} \quad i(t) = A e^{(-1/RC)t} \quad \text{what is } A?$$

we return to the original equation:

Initially $v_C = v_0$ at time $t=0$. Therefore $i(0) = \frac{v_C}{R} = \frac{v_0}{R}$
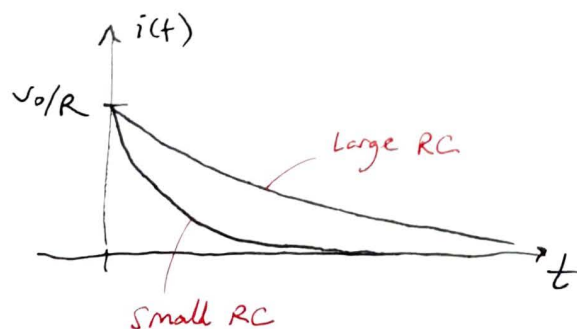
$$i(0) = A e^{-1/RC \cdot 0} = A = \frac{v_0}{R} \quad \Rightarrow \quad i(t) = \frac{v_0}{R} e^{-\frac{t}{RC}}$$




$s + \frac{1}{RC} = 0$ is said to be the characteristic equation of the system.

The product $R \cdot C$ is called time constant. ($\tau = RC$)

Some features of Ae^{st} :

$x = Ae^{-t/\tau}$. The initial slope of x is $\left. \frac{dx}{dt} \right|_{t=0} = -\frac{A}{\tau}$

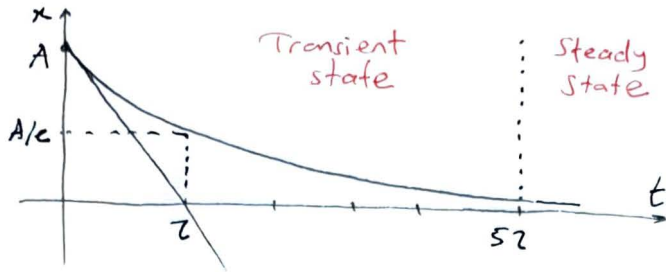


$$x(0) = A$$

$$x(\tau) = \frac{A}{e}$$

Since $e^{-5} = 0.0067$ is very small

It's common to assume that for $t > 5\tau$ the function is zero. So system is said to have completed transient response in 5τ time units


Step response:

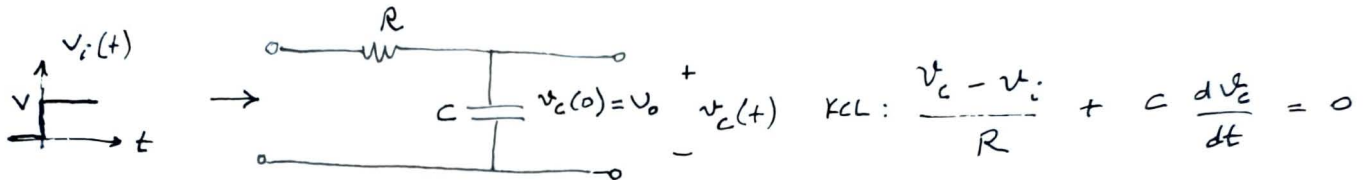

$$V_i = V \cdot u(t)$$

$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$$

Initially the circuit is:

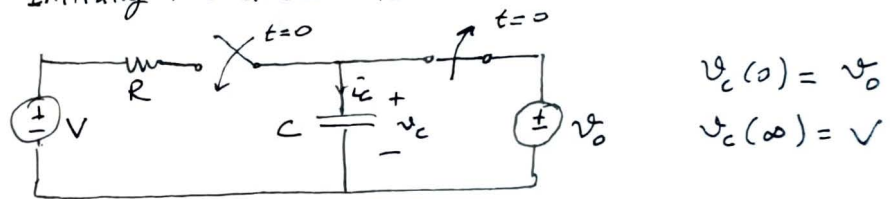


$$V_c(0) = V_0$$

$$V_c(\infty) = V$$

So we can write: $V_c = V + Ae^{-t/RC}$, $V_c(0) = V_0 \Rightarrow V + A = V_0$

$$V_c(\infty) = V \Rightarrow A = \underline{V_0 - V}$$


$$V_c = V + (V_0 - V)e^{-t/RC}$$

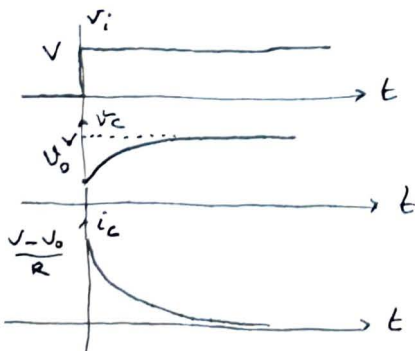

$$V_c = \underbrace{V}_{\text{steady state output}} + \underbrace{(V_0 - V)e^{-t/RC}}_{\text{transient output}}$$

$$i_c = C \frac{dV_c}{dt} = \frac{V - V_0}{R} e^{-t/RC}$$

Analysis of R-L circuit

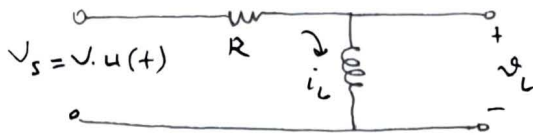

Laplace Transforms

$f(t) \rightarrow$	$F(s)$
$A u(t)$	A/s
$f'(t)$	$sF(s) - f(0)$
e^{-at}	$\frac{1}{s+a}$
$f''(t)$	$s^2 F(s) - s f(0) - f'(0)$
$\sin(at)$	$\frac{a}{s^2 + a^2}$
$\cos(at)$	$\frac{s}{s^2 + a^2}$
$a t u(t)$	A/s^2

$$-V_s + i_L \cdot R + L \frac{di_L}{dt} = 0$$

$$-\frac{V}{s} + I_L(s) \cdot R + L (s I_L(s) - i_L(0)) = 0$$

$$I_L \cdot R + L s I_L = V/s$$

$$s \cdot I_L (R + sL) = V \Rightarrow I_L = \frac{V}{s(R + sL)}$$

$$I_L(s) = \frac{V}{s(R + sL)} = \frac{A}{s} + \frac{B}{R + sL}$$

$$\frac{AR + AsL + Bs}{s(R + sL)} = \frac{V}{s(R + sL)} \Rightarrow$$





$$s(AL + B) + AR = V \Rightarrow A = \frac{V}{R} \quad B = -\frac{VL}{R}$$

$$I_L(s) = \frac{V/R}{s} - \frac{VL/R}{R + sL} = \frac{V/R}{s} - \frac{V/L}{R/s + L}$$

inv. Laplace transform : $i_L(t) = \frac{V}{R} - \frac{V}{R} e^{-\frac{R}{L}t}$

$$v_L = L \cdot \frac{di_L}{dt} = L \left(-\frac{V}{R} \right) \cdot \left(-\frac{R}{L} \right) e^{-\frac{R}{L}t} = V e^{-\frac{R}{L}t}$$

Intuitive analysis:

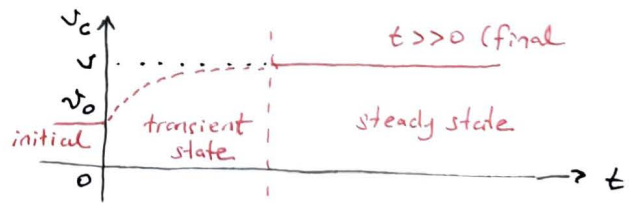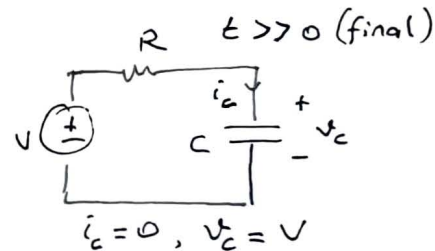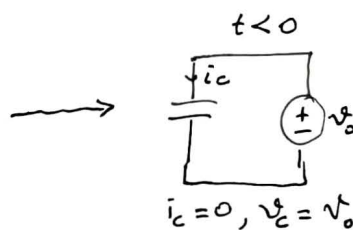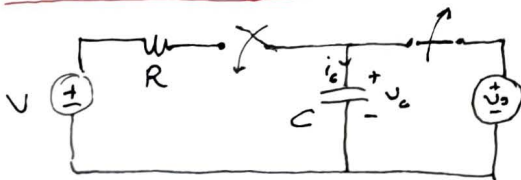


$$v_C = \text{initial value} e^{-t/\text{time constant}} + \text{final value} (1 - e^{-t/\text{time constant}})$$

$$v_C = v_0 e^{-t/RC} + V(1 - e^{-t/RC}) = V + (v_0 - V) e^{-t/RC}$$

steady state component

transient component

Exercise 10.18 (Pg. 572)

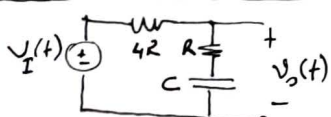

Find the characteristic equation. Assume C is initially charged to 1 volt. Plot $v_0(t)$.